

Course: CSE251 Electronic Circuits

Expt No.: 6

Title: Measurement of Parameters and I-V characteristics of an N-channel MOSFET

Objectives:

1. To measure the threshold voltage V_t and the process transconductance K_n of an N-channel enhancement type MOSFET.
2. To measure the I-V characteristics (I_D vs. V_{DS}) of an N-channel enhancement type MOSFET.

Circuit Diagram:

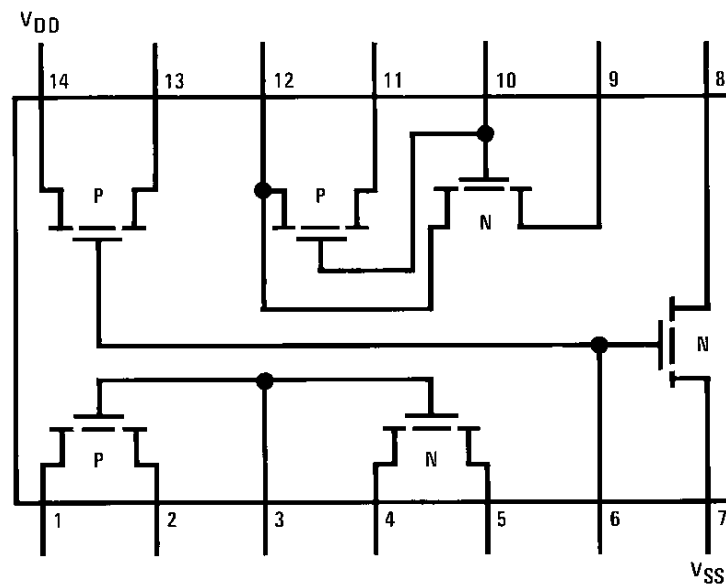


Figure 1. Pin diagram of CD4007C IC.

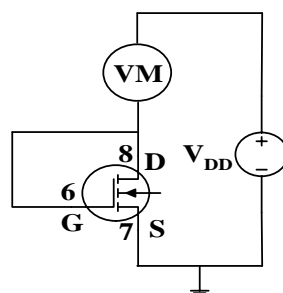


Figure 2. Circuit for measurement of V_t and K_n of an NMOSFET.

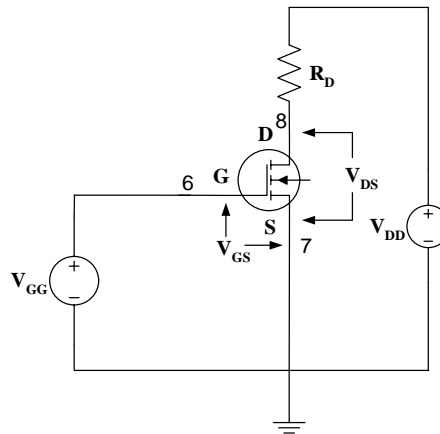


Figure 3. Circuit for measurement of I-V characteristics of an NMOSFET.

Equipments and Components Needed:

1. Digital trainer board
2. DC power supply
3. Digital multimeter
4. DC Voltmeter
5. CD4007C IC (1 pc)
6. Resistor (1K Ω 1 pc)
7. Breadboard
8. Connecting wires

Lab Procedure:

MEASUREMENT OF V_t AND K_n :

1. Measure the resistance and connect the circuit as shown in Figure 2. Note that a voltmeter (VM) is in series with the drain and V_{DD} ; and **G** and **D** are shorted. **Use the pin numbers as shown in Figure 2.**
2. Set V_{DD} to 10V from the DC power supply unit and measure the reading of the voltmeter. The threshold voltage $V_t = V_{DD} - \text{VM reading}$.
3. Now replace the voltmeter by 1K Ω resistance and measure the voltage drop across the resistance. Divide it by the resistance to get I_D . Measure V_{GS} and calculate the process transconductance from $K_n = 2I_D/(V_{GS}-V_t)^2$.

MEASUREMENT OF I-V CHARACTERISTICS:

4. Connect the circuit as shown in Figure 3 and set $V_{GG} = V_t + 1V$ from the trainer board variable power supply.
5. Use the DC power supply unit as V_{DD} . Now change V_{DD} from 0 and measure V_{DS} and V_{RD} (voltage across R_D resistance). Calculate I_D from $I_D = V_{RD}/R_D$. Take around 15 data up to $V_{DS} = 7V$. **Be careful so that V_{DD} does not exceed 15V.**
6. Set V_{GG} to $V_t + 2V$ and $V_t + 3V$ and repeat step 5.
7. Have the datasheet signed by your instructor.

Post-Lab Report Questions:

1. You have V_t and K_n . Note that here K_n is equivalent to $K'_n(W/L)$ of the text. For three V_{GG} ($V_{GG} = V_{GS}$) values of Figure 3, use the linear (triode) and saturation current expressions to tabulate the I_D for each V_{DS} and plot the I_D - V_{DS} curves using your calculated and experimental data on the same graph. Use MATLAB for plotting.

$$I_D = K_n \left[(V_{GS} - V_t) V_{DS} - V_{DS}^2 / 2 \right] \text{linear}$$

$$I_D = (K_n / 2) (V_{GS} - V_t)^2 \text{saturation}$$

2. Write your observation and comments on the calculated and experimental graphs, especially in the saturation regions.
3. For $V_{GG} = V_t + 3V$, take two experimental data points in saturation and calculate the slope. From the slope, obtain output resistance r_o .
4. Simulate the circuit shown in Figure 3 using PSPICE. For simulation use MbreakN3 MOSFET and DC sweep analysis with nested loop for the three different values of V_{GG} . To set the parameters, double click on MbreakN3 and set W and L to 1E-6 (1 μ m). Now select MbreakN3 (it will turn red) and go to Edit \rightarrow Model \rightarrow Edit Instance Model (Text). Delete everything in the appeared window and write the followings (put your values of V_t and K_n) and click OK.

```
.MODEL MbreakN3 NMOS  
LEVEL = 3  
VTO = 1.8  
KP = 100E-6
```