



Lab-report:06

Course Name: Electronic Circuits

Course Code: CSE 251

Section No: 01

Name of experiment: Measurement of Parameters and I-V characteristics of an N-channel MOSFET.

Submitted To:

Touhid Ahmed

Lecturer,

Department of Computer Science and Engineering

East West University

Submitted by:

Student's ID: 2020-3-60-012

Student's Name: Sadia Islam Prova

Student's ID: 2020-3-60-034

Student's Name: Md. Dil Monsur Khan

Student's ID: 2020-3-60-035

Student's Name: Md. Iftekhar Alam Sarkar

Date of submission: 08-05-2022

Objectives:

1. To measure the threshold voltage V_t and the process transconductance K_n of an N-channel enhancement type MOSFET.
2. To measure the I-V characteristics (I_D vs. V_{DS}) of an N-channel enhancement type MOSFET.

Theory:

MOSFET is a metal oxide semiconductor that is under the category of the field-effect transistor (FET). These transistors are widely used under the varieties of the applications relating to the amplification and the switching of the devices. Because of its fabrications MOSFET's are available in smaller sizes.

N-channel MOSFET:

N-channel MOSFET is a type of metal oxide semiconductor field-effect transistors (FET). MOSFET transistor operation is based on the capacitor. This type of transistor is known as an insulated gate field-effect transistor (IGFET).

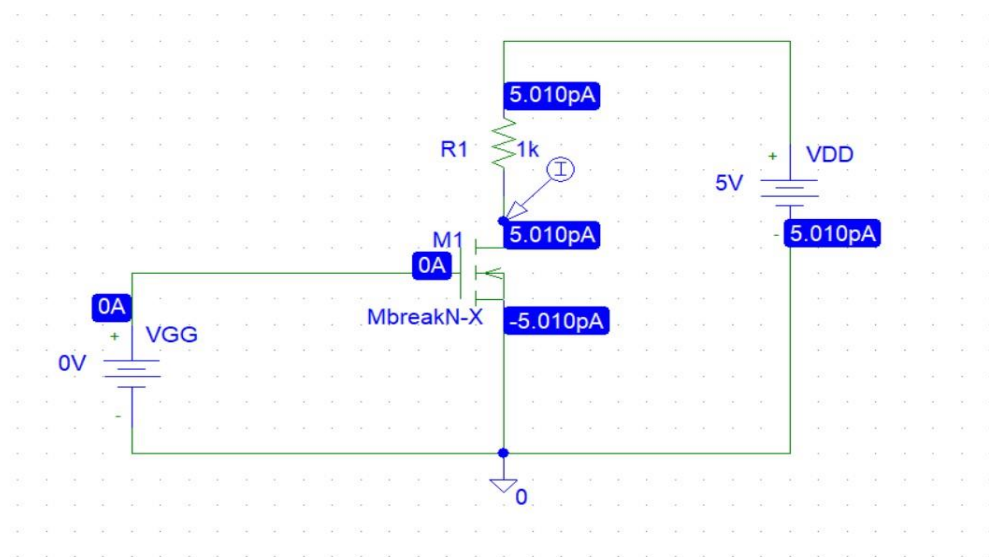
Circuit Diagram:

Figure 01: N-channel MOSFET

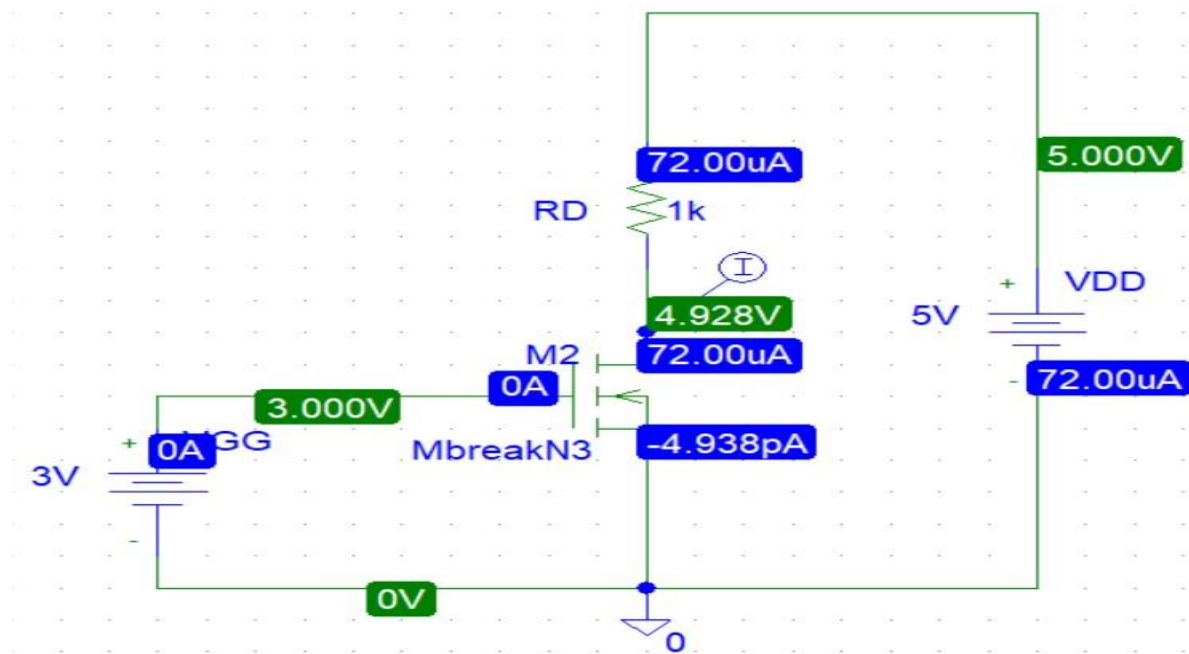
ID-VGS Characteristics:

Figure 02: N-channel MOSFET

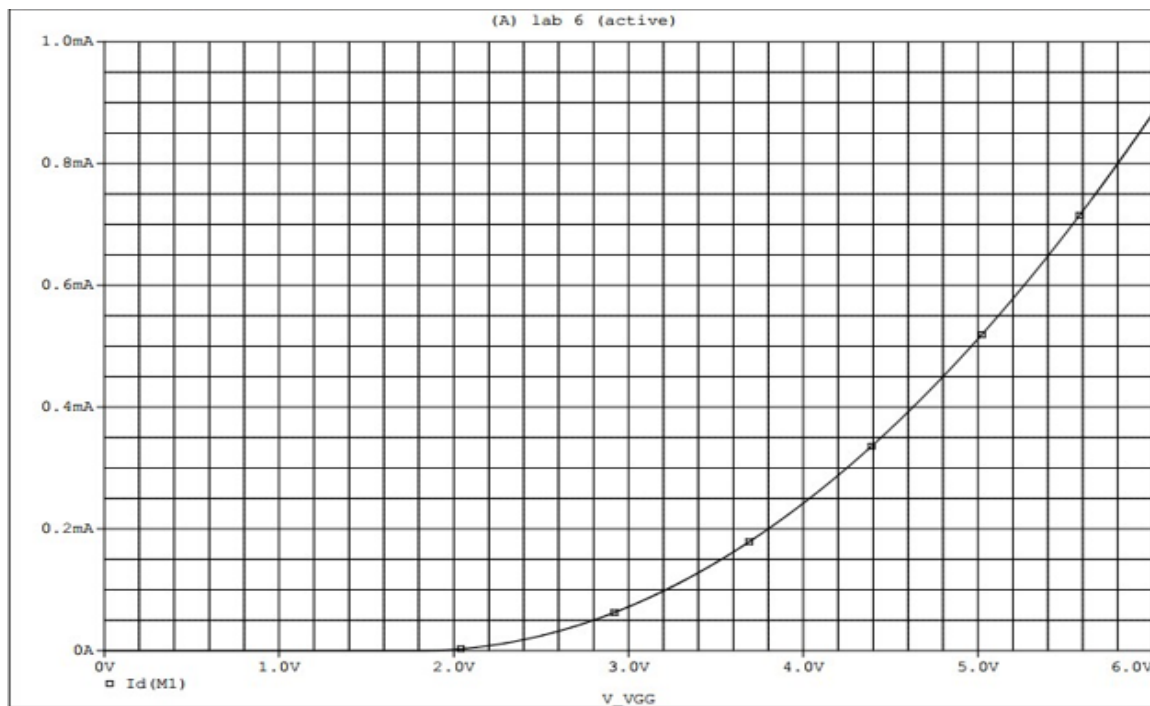


Figure 03: ID-VGS Characteristics

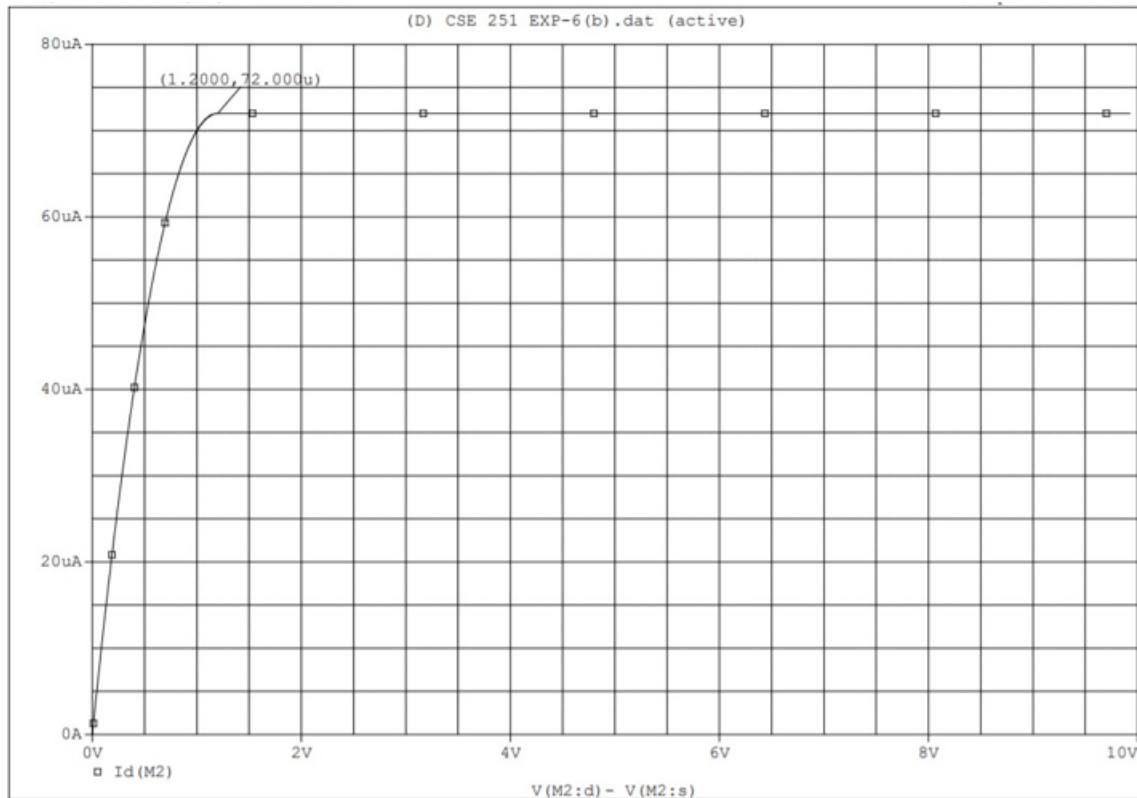


Figure 04: ID-VGS Characteristics

Here, Edge of saturation is 1.2;

If the transition is greater than 1.2 it will operate in saturation region

And, If the transition is less than 1.2 then it will operate in triode region.


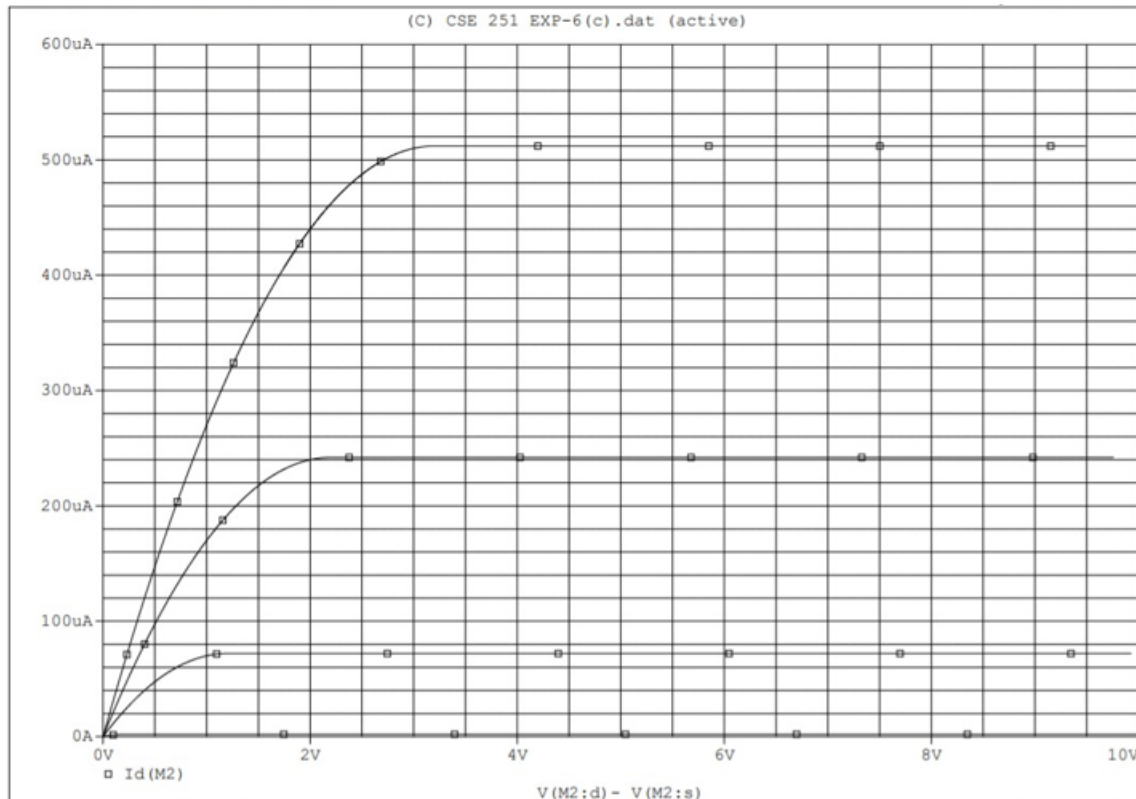


Figure 05: ID-VDS Characteristics for multiple VGS

Equipments and Components needed:

1. Digital trainer board
2. DC power supply
3. Digital multimeter
4. DC voltmeter
5. CD4007C IC (1 PC)
6. Resistor ($1\text{ k}\Omega$ 1 pc)
7. Breadboard
8. Connecting wires

Physical experiment:

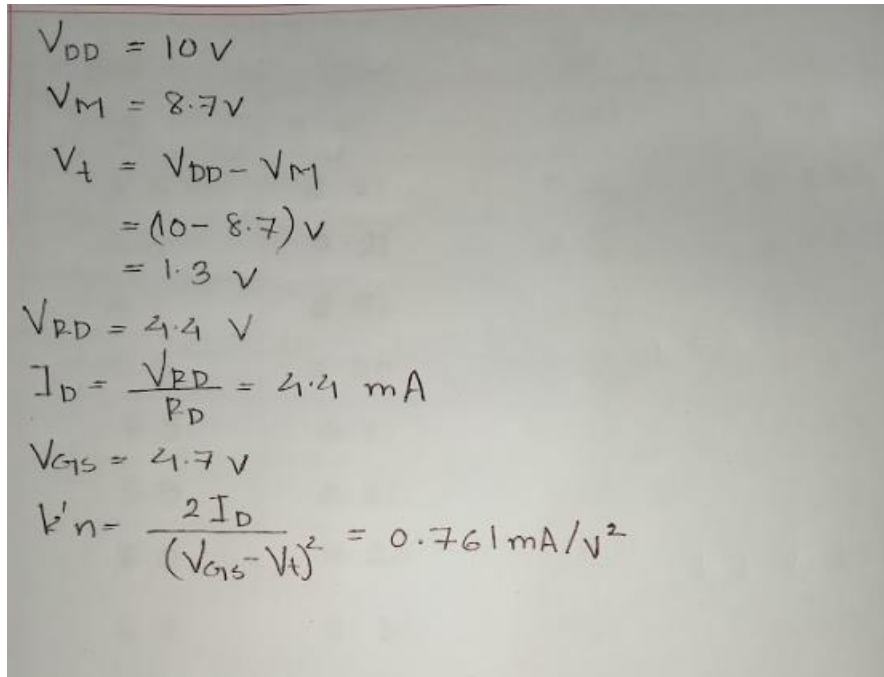

Handwritten calculations on a piece of paper:

$$\begin{aligned}V_{DD} &= 10\text{ V} \\V_M &= 8.7\text{ V} \\V_t &= V_{DD} - V_M \\&= (10 - 8.7)\text{ V} \\&= 1.3\text{ V} \\V_{RD} &= 4.4\text{ V} \\I_D &= \frac{V_{RD}}{R_D} = 4.4\text{ mA} \\V_{GS} &= 4.7\text{ V} \\k'_n &= \frac{2I_D}{(V_{GS} - V_t)^2} = 0.761\text{ mA/V}^2\end{aligned}$$

V_{DD}	V_{RD}	I_D	V_{DS}
3	0.21	0.21	2.75
3.5	0.21	0.21	3.286
4.0	0.21	0.21	3.77
4.1	0.91	0.91	4.11
4.5	0.20	0.20	4.2
5.0	0.21	0.21	4.75
5.5	0.21	0.21	5.26
6.0	0.22	0.22	5.73
6.3	0.24	0.24	5.911
6.5	0.26	0.26	6.271
6.7	0.28	0.28	6.44
6.8	0.29	0.29	6.61
7.0	0.22	0.22	6.703
7.2	0.24	0.24	7.102
7.4	0.28	0.28	7.43

Discussion:

This experiment is carried out both in a physical laboratory and in a virtual environment using PSpice. Because the magnitudes were not interrupted in PSpice, the trials were considerably easier to carry out. As a result, the predicted and experimental values were similar. However, there is a discrepancy while the experiment was carried out physically