



Lab-report:01

Course Name: Electronic Circuits

Course Code: CSE 251

Section No: 01

Name of experiment: I-V characteristics and Modeling of Forward Conduction of a Diode

Submitted To:

Touhid Ahmed

Lecturer,

Department of Computer Science and Engineering

East West University

Submitted by:

Student's ID: 2020-3-60-012

Student's Name: Sadia Islam Prova

Date of submission: 08-05-2022

Objectives:

1. To measure the I-V characteristics of forward conduction of a p-n junction diode.
2. To determine the models of forward conduction of a p-n junction diode.

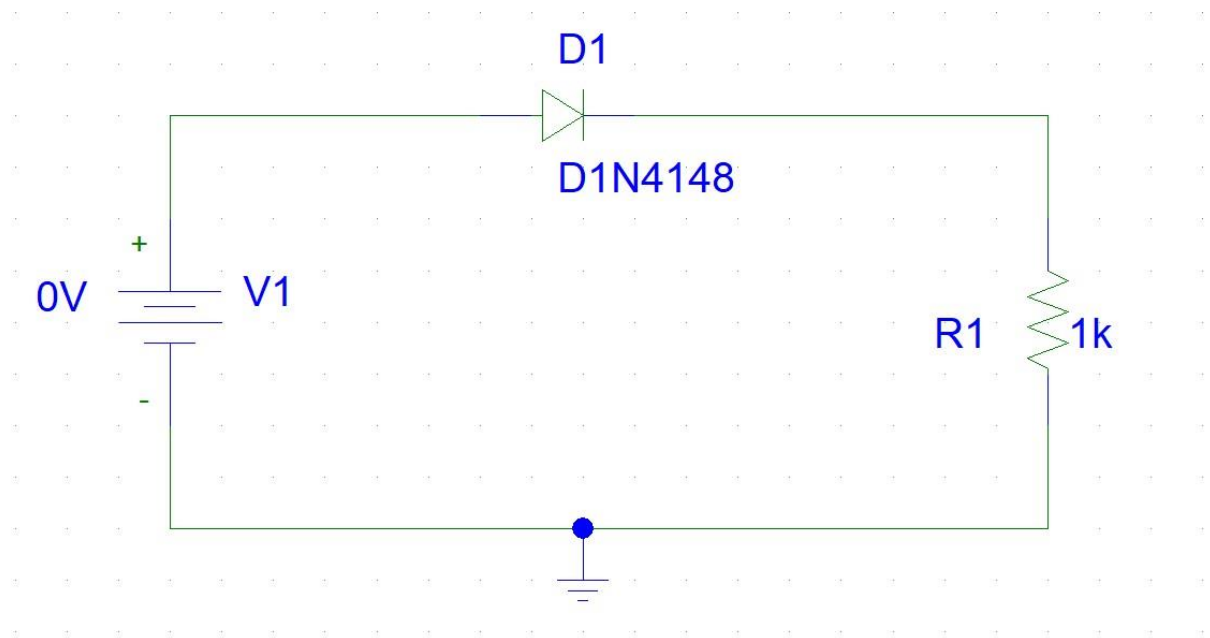
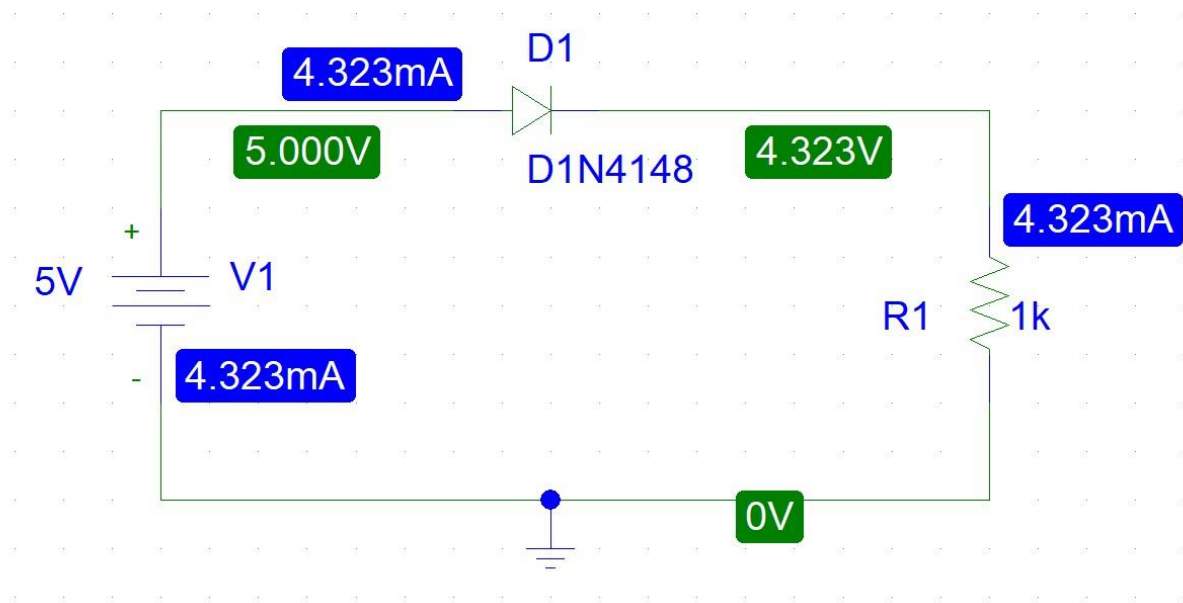
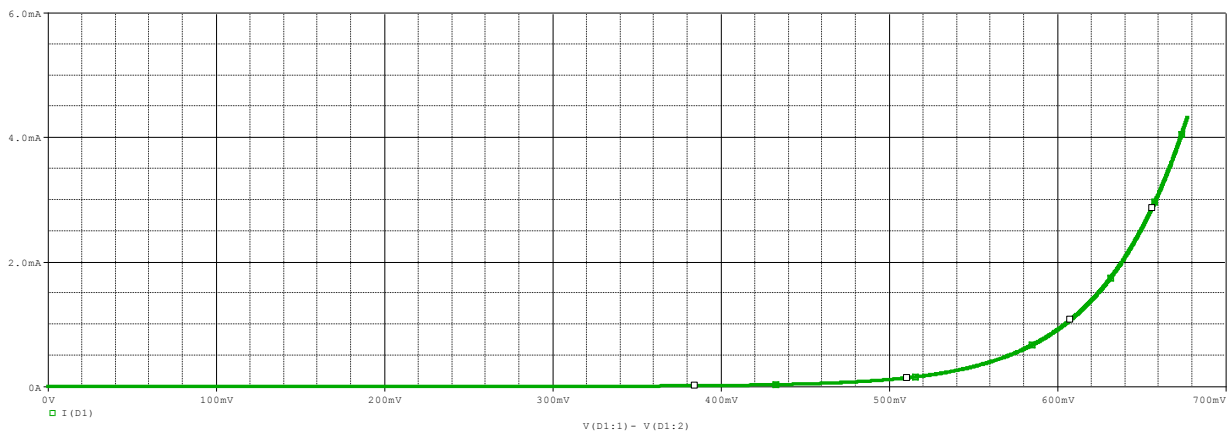
Circuit Diagram:

Figure 01: Circuit set up to measure forward bias I-V characteristics of a diode

Answer to the question no: 01**Figure 02:** Circuit Simulation of forward biased Silicon PN junction diode**Answer to the question no: 02****Figure 03:** Model Silicon PN junction Diode I-V characteristics in forward bias

Answer to the question no: 03

At $I = (X+1) \text{ mA} = 3\text{mA}$; Here $X=2$ (Last digit of my Id)

We know,

$$I_D = I_S \exp[V_D / nV_T]$$

$$\Rightarrow P_1 = I_{D1} = I_S \exp[V_{D1} / nV_T] \dots \dots \dots (1)$$

$$\Rightarrow P_2 = I_{D2} = I_S \exp[V_{D2} / nV_T] \dots \dots \dots (2)$$

(2) \div (1) \Rightarrow

$$I_{D2} / I_{D1} = I_S \exp[V_{D2} / nV_T] / I_S \exp[V_{D1} / nV_T]$$

$$\Rightarrow I_{D2} / I_{D1} = \exp [V_{D2} - V_{D1} / nV_T]$$

$$\Rightarrow \ln(I_{D2} / I_{D1}) = V_{D2} - V_{D1} / nV_T$$

$$\Rightarrow n = V_{D2} - V_{D1} / V_T \times \ln(I_{D2} / I_{D1}) \dots \dots \dots (3)$$

From equation(1);

$$I_S = I_{D1} \exp[-V_{D1} / nV_T] \dots \dots \dots (4)$$

$$I_{D1} = 2.8502 \text{ mA}$$

$$V_{D1} = 656.427 \text{ mV}$$

$$I_{D2} = 3.3674 \text{ mA}$$

$$V_{D2} = 664.233 \text{ mV}$$

$$\text{Now, } n = (V_{D2} - V_{D1}) / V_T \ln(I_{D2}/I_{D1})$$

$$= (664.233 - 656.427) / \{ 26 \text{ mV} \times \ln(3.367 / 2.850) \}$$

$$= 1.805$$

$$\begin{aligned}
 I_S &= I_{D1} \exp[-V_{D1} / nV_T] \\
 &= 2.850 \times 10^{-3} \exp[-656.427 / 1.805 \times 26] \\
 &= 2.40 \times 10^{-9} \text{ A}
 \end{aligned}$$

DC Resistance:

$$\begin{aligned}
 I_D &= 3.3674 \text{ mA} \\
 V_D &= 664.233 \text{ mV}
 \end{aligned}$$

$$\begin{aligned}
 R_D &= V_D / I_D \\
 &= 664.233 \text{ mV} / 3.367 \text{ mA} \\
 &= 197.277 \Omega
 \end{aligned}$$

Average AC Resistance:

$$\begin{aligned}
 I_{D1} &= 2.8502 \text{ mA} \\
 V_{D1} &= 656.427 \text{ mV} \\
 I_{D2} &= 3.3674 \text{ mA} \\
 V_{D2} &= 664.233 \text{ mV}
 \end{aligned}$$

$$\begin{aligned}
 R_{AC} &= V_{D2} - V_{D1} / I_{D2} - I_{D1} \\
 &= 664.233 - 656.427 / 3.367 - 2.850 \\
 &= 15.098 \Omega
 \end{aligned}$$

Dynamic AC Resistance:

$$I_D = 3.367 \text{ mA}$$

$$n = 1.805$$

$$V_T = 26 \text{ mV}$$

$$r = nV_T / I_D$$

$$= (1.805 \times 26) / 3.367$$

$$= 13.938 \, \Omega$$

Answer to the question no:04

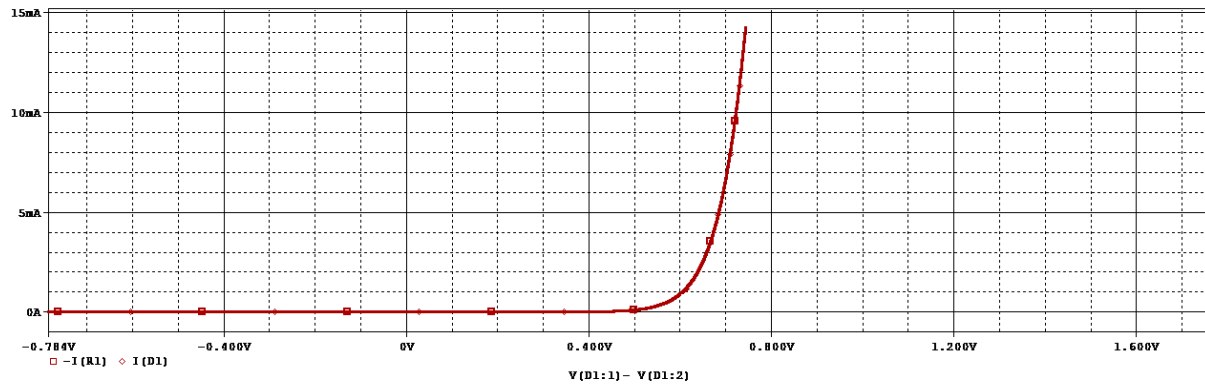


Figure 04: Forward region in Diode I-V characteristics

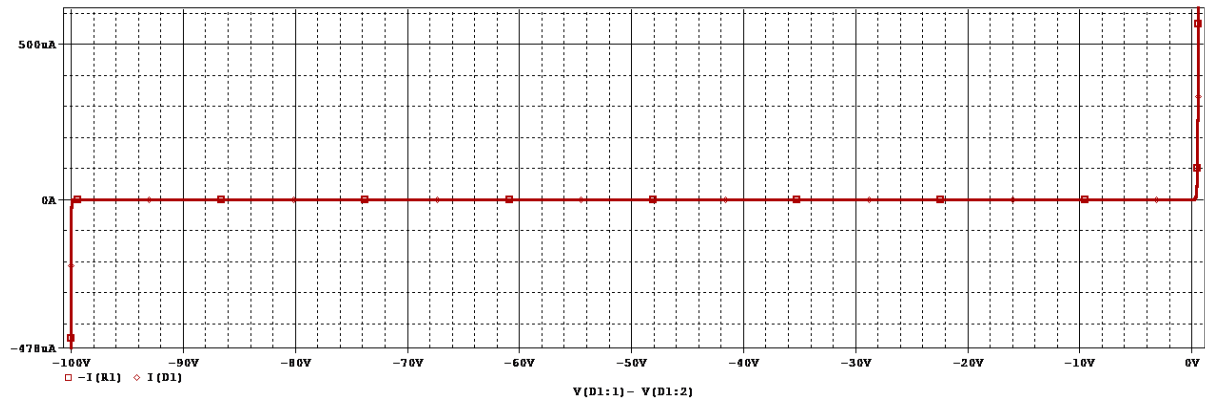


Figure 05:Reverse region in Diode I-V characteristics.

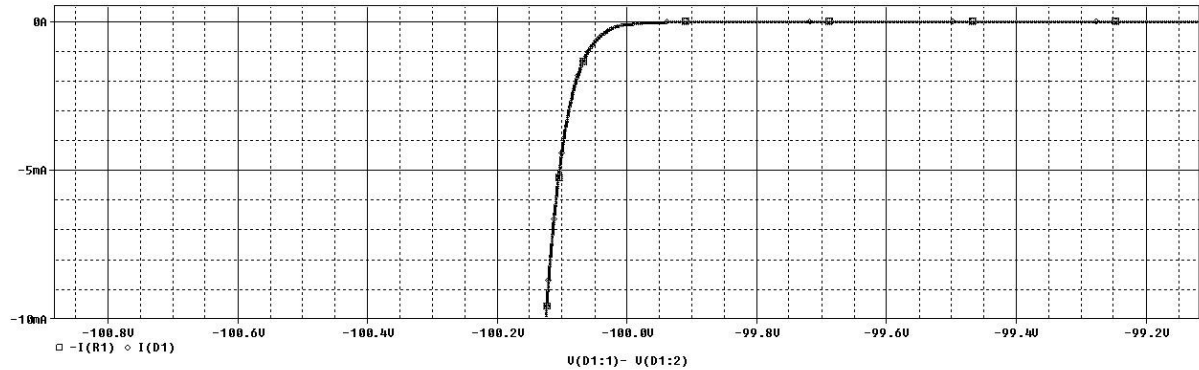


Figure 06: Zener region in Diode I-V characteristics

Discussion:

In forward conduction, an ideal diode works like a short circuit, but in practice, it consumes some voltage to function like a short circuit, but it still doesn't act like a short circuit completely due to leak voltage. Diodes prevent currents from flowing in the wrong direction, as we discovered in our experiment. The I vs. V features teach us about forward and backward situation. Here, all the graphs & values are calculated in the PSpice simulation software.

